 

Simulation vs. Synthesis

Execution Models for VHDL Programs


- Two classes of execution models govern the application of VHDL programs
- For Simulation
 - Discrete event simulation
 - Understanding is invaluable in debugging programs
- For Synthesis
 - Hardware inference
 - The resulting circuit is a function of the building blocks used for implementation
 - Primitives: NAND vs. NOR
 - Cost/performance

Simulation vs. Synthesis




- Simulation and synthesis are complementary processes

Simulation of Digital Systems

 

- Digital systems are modeled as the generation of events – value transitions – on signals
- Discrete event simulations manage the generation and ordering of events
 - Correct sequencing of event processing
 - Correct sequencing of computations caused by events


Discrete Event Simulation: Example

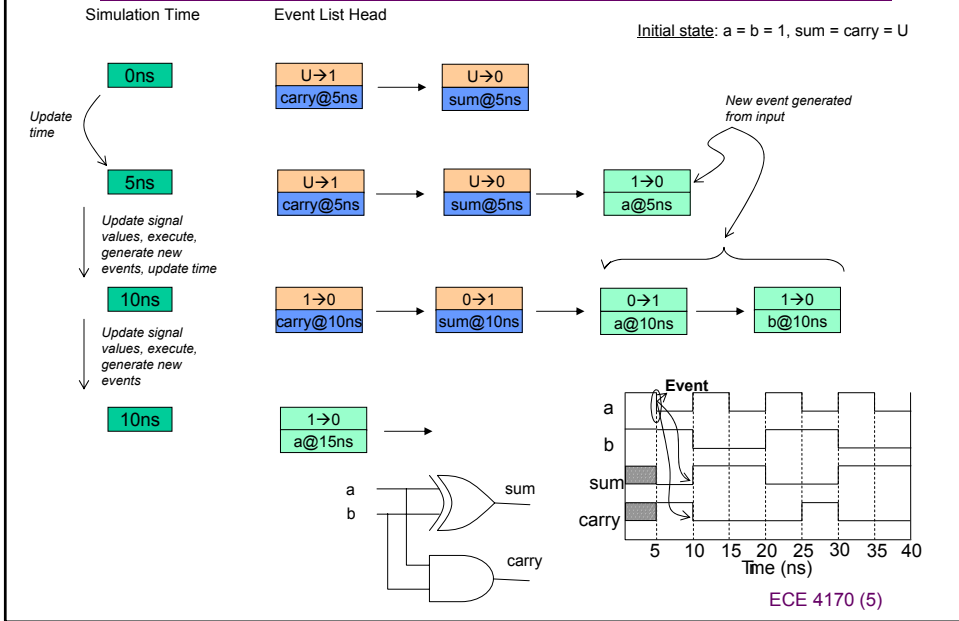

Discrete Event Simulation


- Management of simulation time: ordering of events
- Two step model of the progression of time
 - Evaluate all affected components at the current time: events on input signals
 - Schedule future events and move to the next time step: the next time at which events take place

Simulation Modeling

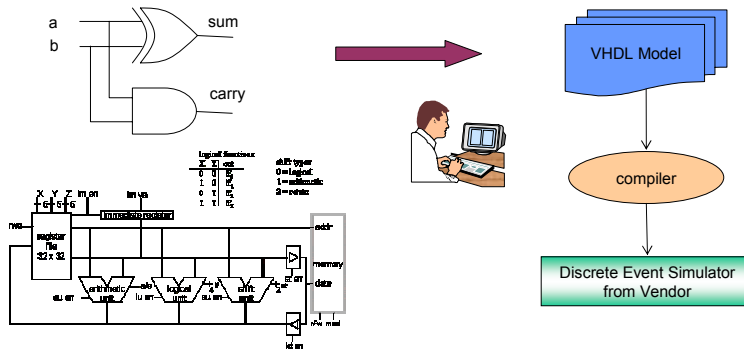

- VHDL programs describe the generation of events in digital systems
- Discrete event simulator manages event ordering and progression of time
- Now we can quantitatively understand accuracy vs. time trade-offs
 - Greater detail → more events → greater accuracy
 - Less detail → smaller number of events → faster simulation speed


Synthesis and Hardware Inference

 

- Both processes can produce very different results!

Inferring Combinational Logic

 
```
--
-- pseudo code for a single bit arithmetic/ logic unit
--
s1 <= in1 and in2;
s2 <= in1 or in2;
s3 <= in1 xor in2; -- perform the sum operation
c_out <= (in1 and c_in) or (in1 and in2)
           or (in2 and c_in);
out <= s1 when sel = "00" else
      s2 when sel = "01" else
      s3 when sel = "10" else
      '0';
```



- Each statement implies a logic component


Inferring Sequential Logic
 
```
--
-- a simple conditional code block
--
if (sel = '0') then
    z <= in1 nor in2;
end if;
```




- Inference of sequential components is more subtle
 - All possible execution paths through the code must be accounted for
- Results are very sensitive to the manner in which code is written
- Inferences of latches vs. flip flops

Optimization

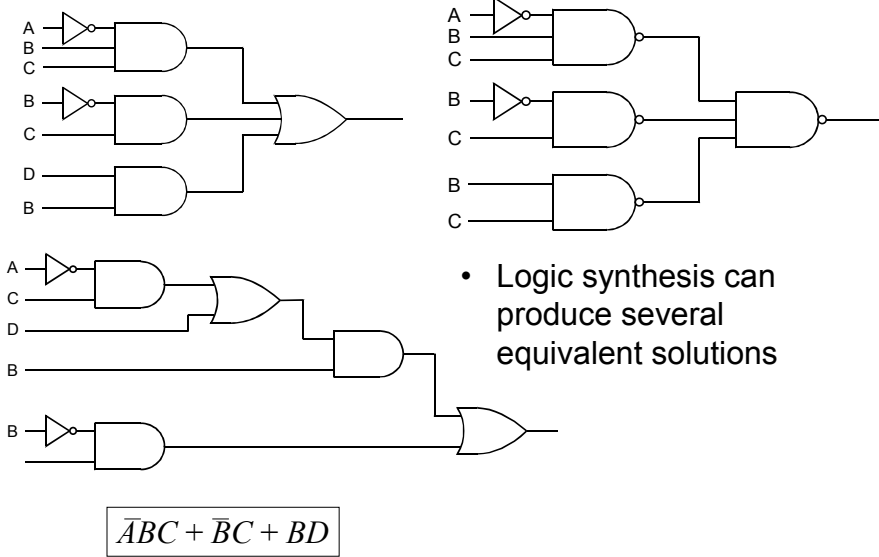


- Logic synthesis can produce several equivalent solutions

 Field Programmable Gate Arrays: Principles




- The chip is tiled with Configurable Logic Blocks (CLBs)
 - each block can “implement” a few gates and flip flops
- An interconnect switching matrix is interleaved with this array of CLBs
- Usage: partition, place, and route a design

Inside a Xilinx Configurable Logic Block

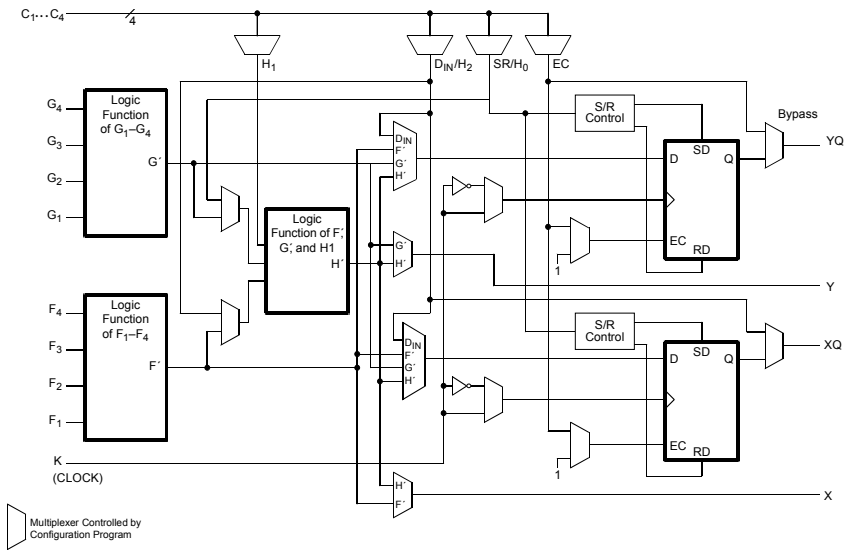


ECE 4170 (13)

Inside a Xilinx IO Block

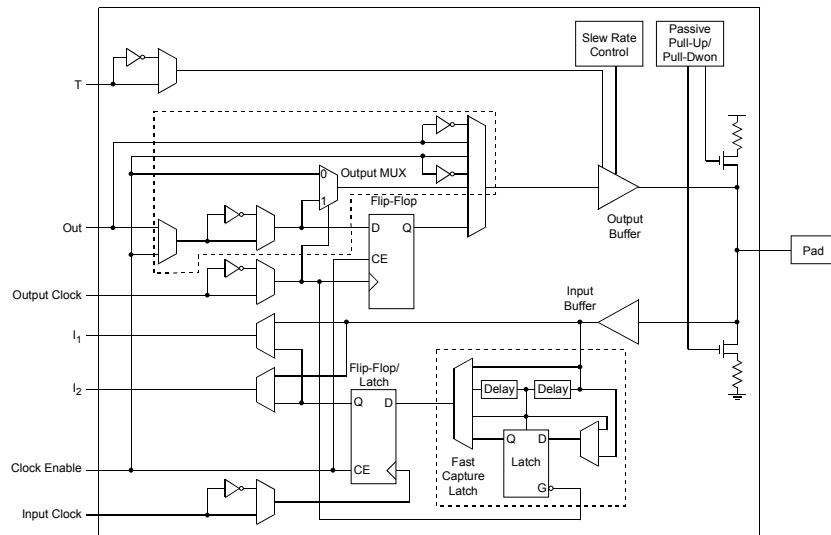

ECE 4170 (14)


Implementing Digital Circuits in a CLB

 

- Boolean functions are implemented as look-up tables
- Combinations of lookup tables implement multivariable functions
- Implementation of behavior
- Sequential circuits use CLB latches/flip flops

ECE 4170 (15)

Wiring Resources

 


- Optimize signal delay
- “Chip length” signals can be configured as buses
- Global nets for low skew clocks and reset signals

ECE 4170 (16)

- Carry chains between columns of CLBs
- Configuration of CLB RAM as
 - Memories rather than lookup tables
 - Shift registers (Xilinx Virtex 5)
- Core generators
 - Optimized libraries of components
 - Vendor supplied
- Configuration bit stream for configuring a design
 - What about editing the bit stream directly!


- Configuration bits for CLBs
 - bits for loading the LUTs
 - bits for configuring the flip flops
 - bits for setting multiplexors
- Configuration bits for the switch matrix
 - Connecting horizontal and vertical lines
 - Tri-state devices within the CLBs
- Configuration bits for the IOBs
 - IO clocks
 - storage vs. direct “access” to the pin
- Equivalent concepts for all vendors

Heterogeneous FPGAs: The Xilinx Virtex 5

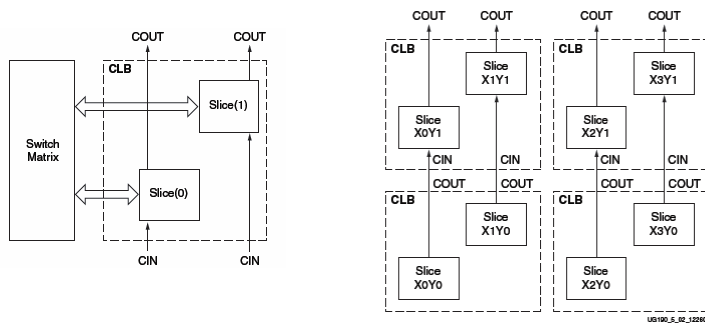


- Basic building block remains the same
- Substrate augmented with “hard cores”

The Basic Virtex 5 Slice

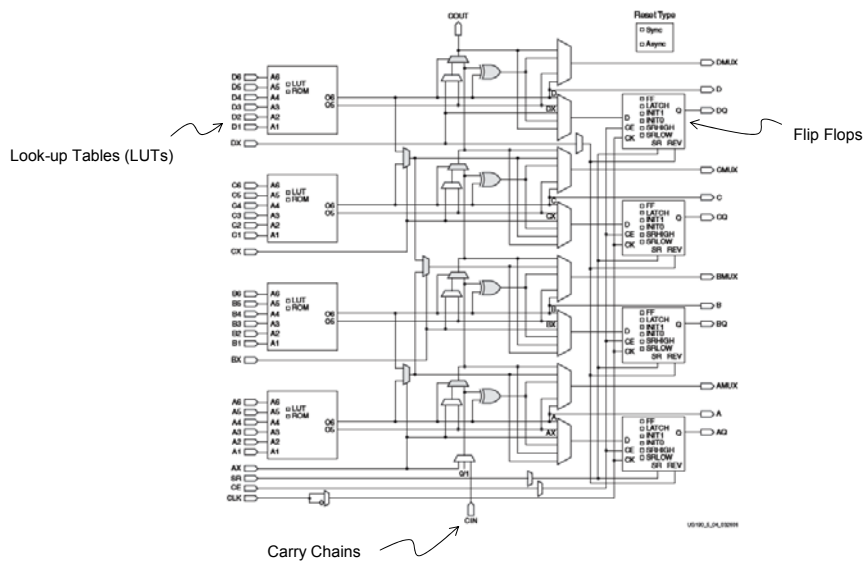


Customized Virtex 5 Slice

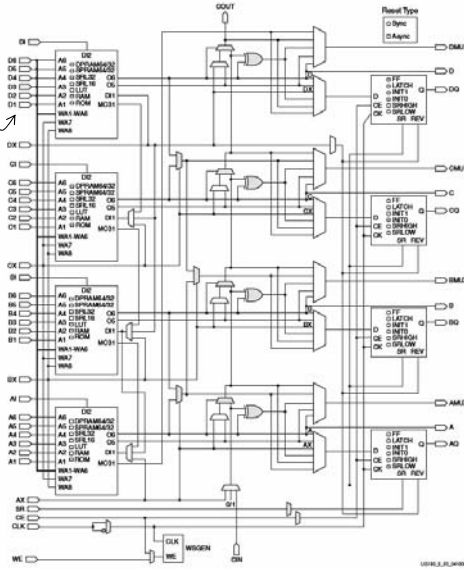Can be configured as Block RAM or Shift register



ECE 4170 (21)


A DSP Slice

 

- Product families are customized with differing ratios of slice types to address different market segments

ECE 4170 (22)

A Simplified Design Flow

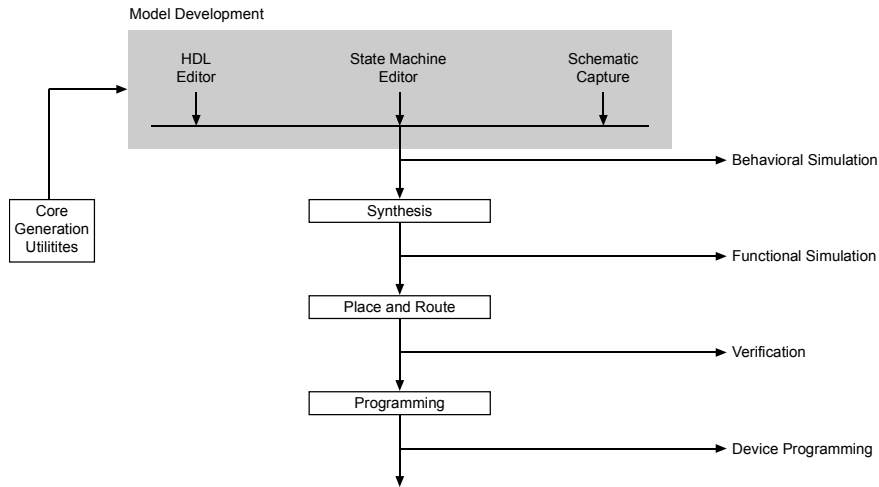

ECE 4170 (23)

Summary

- VHDL is used to describe digital systems and hence has language constructs for key attributes
 - Events, propagation delays, and concurrency
 - Timing, and waveforms
 - Signal values and use of multiple drivers for a signal
- VHDL has an underlying discrete event simulation model
 - Model the generation of events on signals
 - Built in mechanisms for managing events and the progression of time
 - Designer simply focuses on writing accurate descriptions

ECE 4170 (24)