 


Observations for other Positive Edge-Triggered D-FF




positive edge-triggered TSPC D-flip flop (non-split output)

Need to analyze for clock = 0 (master sampling, slave holding), clock 0 → 1, clock = 1:

clock	D	X	Y	\bar{Q}
0	0	1	1	\bar{Q}_{old}
0	1	0	1	\bar{Q}_{old}

 Need to force \bar{Q}_{old} to a "1". Can do it by → → → → → → → → →




Check other cases:

clock	D	X	Y	\bar{Q}
0 → 1	0	$X_{old} (= 1)$	0	1
0 → 1	1	$X_{old} (= 0)$	$Y_{old} (= 1)$	0

For the above case where clock is going 0 → 1 and D = 0, no reset is needed. In the second case above where clock is going 0 → 1 and D = 1, we need to force Y_{old} to be a zero when reset is asserted. How to do this?


Here's one way:

 

When clock (\emptyset) = 0 \rightarrow 1, $R = 0$, $\bar{R} = 1$, then forces Y node = 0. Even works when clock = 0, can get rid of p MOS pullup on \bar{Q} output.


Will have to invert R inside of circuit because R is low true, so final transistor count for adding asynchronous low true reset is 4.

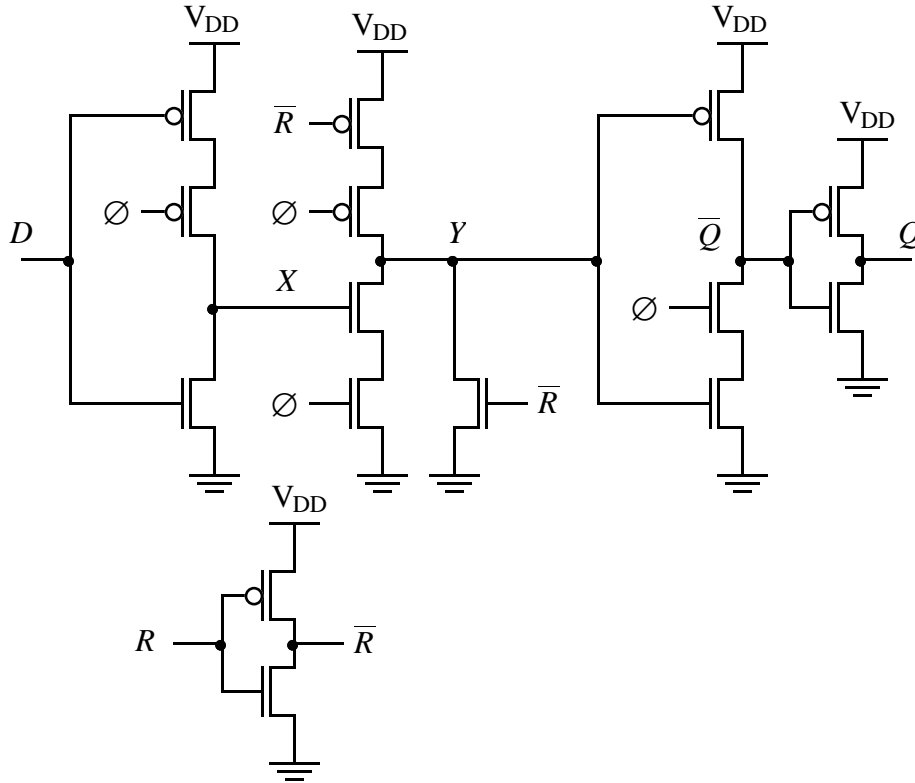Final circuit (positive edge-triggered TSPC *D*-flip flop with asynchronous, low-true reset):




Final transistor count = 15. Recall again that a static *D*-flip flop can require 33 transistors!

Final check →

 
 
$$\begin{aligned}
 X &= X_{\text{old}} & Y &= Y_{\text{old}} \\
 Y &= 0 & \bar{Q} &= 1 \\
 \bar{Q} &= 1
 \end{aligned}$$



$$\begin{aligned}
 X &= \overline{\text{data}} & Y &= 1 \\
 Y &= 0 & \bar{Q} &= \bar{Q}_{\text{old}} = 1 \\
 \bar{Q} &= 1
 \end{aligned}$$