

Q.1

Dec. 2016

a. Several programming techniques the most used ones are :
MUX based, Look-up Table, PAL, EPROM, PLA etc.

1) Mux based programming uses $2 \rightarrow 1$ Multiplexers to implement the gates as a basic unit and build on the technique to build larger functions


Example an EX-OR is built as $A \oplus B$.



2 - Look Up Table represent a function with K -variables in a memory table with one output. It requires 2^k memory location each location is addressed by k bits with $2^k - 1$ MUXes with access time of k MUX + 1 read of memory.

b.

a_1	a_0	b_1	b_0	P_3	P_2	P_1	P_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	0	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	0	0	0	0
1	0	1	1	0	0	0	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	0	0
1	1	1	0	0	0	0	0
1	1	1	1	0	0	0	0

 

The same architecture is used for P_1, P_2 and P_3 with different Memory for P_1, P_2 & P_3


Total Area = $4 * [16 \text{ cells} + 15 \text{ Mux}] = 4 * [16 * 2A + 15A] = 4 * 47 = 188$

Total Delay = $0.5D_{\text{cell}} + 4D_{\text{mux}} = 4.5D$

Q2 Dec 2016

$F = (N-1)^2$ --- N is a 3-bit unsigned number $N = N_2 N_1 N_0$

	N			F						Equivalent Decimal		
	N_2	N_1	N_0	F_6	F_5	F_4	F_3	F_2	F_1			F_0
0	0	0	0	0	0	0	0	0	0	1	1	$F_0 = \sum_m (0, 2, 4, 6) = \bar{N}_0$
1	0	0	1	0	0	0	0	0	0	0	0	$F_1 = \sum_m 0 = 0$
2	0	1	0	0	0	0	0	0	0	1	1	$F_2 = \sum_m (3, 7) = N_1 N_0$
3	0	1	1	0	0	0	0	1	0	0	4	$F_3 = \sum_m (4, 6) = N_2 \bar{N}_0$
4	1	0	0	0	0	0	1	0	0	1	9	$F_4 = \sum_m (5, 6) = N_2 (N_1 \bar{N}_0 + \bar{N}_1 N_0)$
5	1	0	1	0	0	1	0	0	0	0	16	$F_5 = \sum_m (7) = N_2 N_1 N_0$
6	1	1	0	0	0	1	1	0	0	1	25	
7	1	1	1	0	1	0	0	1	0	0	36	

 

Delay = $2 * 2 = 4ms$


Area = 6 Agate

An Alternative to implement the function by a LUT. But that is requires more delay & Area.

Also it can be implemented by a multiplier using carry save adders as $N^2 = 2N + 1$ but the delay & Area is prohibitive.

 Q3 Dec 2016

This adder has 2 states to remember C There is a Carry
 \bar{C} " " no "



Present state	Next state/output			
	00	01	11	10
$\bar{C} = 0$	0/0	0/1	1/0	0/1
$C = 1$	0/1	1/0	1/1	1/0

Transition Table


C	AB			
	00	01	11	10
0		1		1
1	1		1	

$S = A \oplus B \oplus C$


C	AB			
	00	01	11	10
0			1	
1		1	1	1

$C = AB + AC + BC$

using D FlipFlop

 

or

 

Q4 Dec 2016

Paths to be Considered

- P1 $U_0 \rightarrow U_{10} \rightarrow U_{11}$
- P2 $U_0 \rightarrow U_4 \rightarrow U_5 \rightarrow U_7 \rightarrow U_8$
- P3 $U_0 \rightarrow U_4 \rightarrow U_1 \rightarrow U_2$
- P4 $U_2 \rightarrow U_{10} \rightarrow U_{11}$
- P5 $U_2 \rightarrow U_3 \rightarrow U_6 \rightarrow U_7 \rightarrow U_8$
- P

- P6 $U_8 \rightarrow U_9 \rightarrow U_{10} \rightarrow U_{11}$
- P7 $U_8 \rightarrow U_6 \rightarrow U_7 \rightarrow U_8$
- P8 $U_8 \rightarrow U_5 \rightarrow U_7 \rightarrow U_8$
- P9 $U_8 \rightarrow U_1 \rightarrow U_2$

* } Critical Path
* } with fan out only

We will Consider Fan-Out Only

Combinational Path only

- $C_{P1} = 2 * 0.25 + 0.25 = 0.75 \text{ ns}$
- $C_{P2} = 2 * 0.25 + 0.15 + 2 * 0.1 + 0.25 + 0.25 = 1.4 \text{ ns}$
- $C_{P3} = 2 * 0.25 + 0.15 + 2 * 0.1 + 0.25 = 1.15 \text{ ns}$
- $C_{P4} = 2 * 0.25 + 0.25 = 0.75 \text{ ns}$
- $C_{P5} = 2 * 0.25 + 0.15 + 0.25 + 0.25 = 1.15 \text{ ns}$
- $C_{P6} = 5 * 0.25 + 0.15 + 0.25 = 1.65 \text{ ns}$
- $C_{P7} = 5 * 0.25 + 0.25 + 0.25 = 1.75 \text{ ns}$
- $C_{P8} = 5 * 0.25 + 0.25 + 0.25 = 1.75 \text{ ns}$
- $C_{P9} = 5 * 0.25 + 0.25 = 1.5 \text{ ns}$

} Critical Path

Path Delay = $1.5 + 1.75 + 1 = 4.25 \text{ ns}$

Frequency of operation $\leq \frac{10^9}{4.25} \approx 235 \text{ MHz}$

$K_T = \frac{273 + (40 + 2 * 30)}{273 + 40} = \left(\frac{373}{313}\right)^{1.5} = 1.3$

New frequency of operation $\approx \frac{235}{1.3} \approx 180 \text{ MHz}$



U8 has the highest fan-out

Q5 Dec 2016

There are 3 paths in this circuit:

Path 1 $D_0 \rightarrow \text{XOR} \rightarrow D_0 = 3.65 \text{ ns}$ ✓ Critical Path

Path 2 $D_1 \rightarrow \text{XOR} \rightarrow D_0 = 2.75 \text{ ns}$

Path 3 $D_1 \rightarrow D_1 = 2.2 \text{ ns}$

a) Arrival at Point A = $0.7 + 0.3 * 2 + \cancel{1.5 * 0.1} + 0.1(1.5 + 2) = 1.65 \text{ ns}$;

b) Time period = $\frac{10^9}{200 * 10^6} = 5 \text{ ns}$

Time required for both D_0 & $D_1 = T - t_{su} = 5 - 0.5 = 4.5 \text{ ns}$

Arrival at point $D_0 = 1.65 + 2 = 3.65 \text{ ns}$

$T_{\text{set-up slack}} = 4.5 - 3.65 = 0.85 \text{ ns}$

$T_h \leq t_{cQ} + t_Q - t_{cs} = t_{cQ} + t_Q = 1.65 + 0.3 + 0.2 * 3 + 0.2 = 2.75 \text{ ns}$

Hold time slack = $2.75 - 0.2 = 2.55$

Arrival at point $D_1 = 0.7 + \frac{f_o}{3} * 0.3 + \underbrace{(2 * 1.5 * 3)}_{\text{load}} * 0.1 = 0.7 + 0.9 + 0.6 = 2.2 \text{ ns}$




$T_{\text{setup slack}} = 4.5 - 2.2 = 2.3 \text{ ns}$

$T_h \leq t_{cQ_{\min}} + t_{Q_{\min}} - t_{cs} = 0.7 + (3 * 0.3) + (2 * 1.5 * 3) * 0.1 = 2.2 \text{ ns}$

Hold slack = $2.2 - 0.2 = 2 \text{ ns}$

Path 1 = $0.7 + 4 * 0.3 + (4.5 + 2) * 0.1 + 0.3 + 0.2 + 3 * 0.2 = 3.65$

   Maximum frequency = $\frac{1}{(3.65 + 0.5) \text{ ns}} = 240 \text{ MHz}$



Q6 Dec 2016

* This is only sample of possible answer *

refer to class notes for more detail

MUX

```

library ieee;
use ieee.std_logic.1164.all;
entity MUX is
  Port (D1, D2, C: in std_logic;
        Z: out std_logic);
end MUX;

```

Architecture RTL of MUX is

```

Component AND2 is
  Port (A, B: in std_logic; C: out std_logic); end Component AND2;
Component OR2 is
  Port (A, B: in std_logic; C: out std_logic); end Component OR2;
Component INV is
  Port (A: in std_logic; B: out std_logic); end Component INV;
Signal S1, S2, S3: std_logic;

```

→ For statements → Work ...

Configuration Statements ←

```

Port map statement →
end RTL;

```

Generator

```

library ieee;
use ieee.std_logic.1164.all;
entity Generator is
  Port (A, B, C: out std_logic); end Generator;
Architecture of Behavior of Generator is
  Begin
  P1: Process
  Begin

```

```

    A <= '0'; B <= '0'; C <= '0'; wait for T1 ms;
    → other values of A, B, C with wait statements ←
  End Process P1; end Behavior;

```

```

use ieee.std_logic.1164.all;
entity Test Bench is
  Architecture of TB is
  Component Generator is
  Component MUX is
  Signal S1, S2, S3: std_logic;
  Begin
  Generator Portmap (S1, S2, S3);
  MUX Portmap (S1, S2, S3, Z);
  End TB;

```

```

  Component Generator is
  Component MUX is
  Signal S1, S2, S3: std_logic;
  Begin
  Generator Portmap (S1, S2, S3);
  MUX Portmap (S1, S2, S3, Z);
  End TB;

```