© Zainalabedin Navabi, 1994

PART 2

VHDL_Overview

- A Moore 110 sequence detector
- Behavioral description
- Using process statements
- Top-down design of the sequence detector
- Using available components
- Wiring predefined components
- Wiring from bottom to top
- Generation of data for testbench
- Using procedures
- A simulatable design
- Other VHDL operators

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110_detector

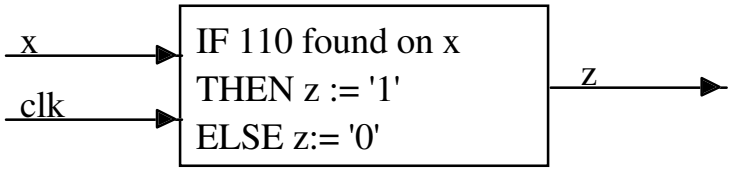

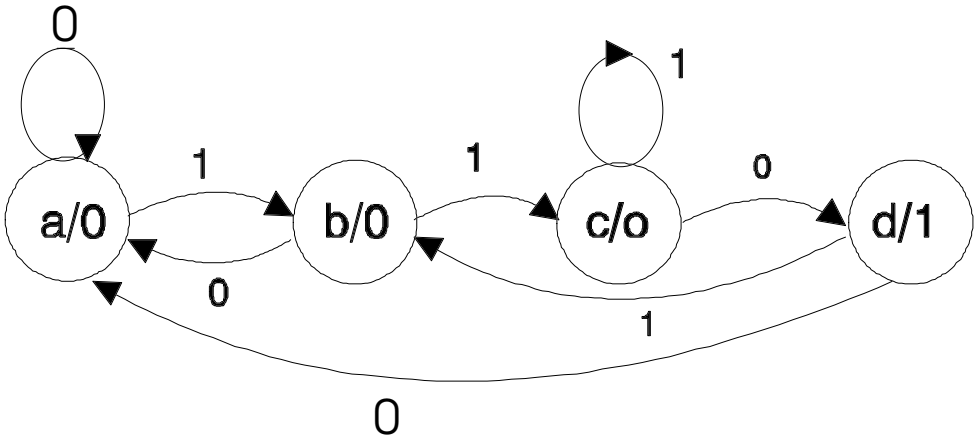

- Design a 110 detector
- Detect 110 on *x*
- Output becomes 1 when found

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110_detector.behavioral

```
ENTITY moore_110_detector IS    PORT (x, clk : IN BIT; z : OUT BIT);
END moore_110_detector;
--
ARCHITECTURE behavioral OF moore_110_detector IS
   TYPE state IS (reset, goto1, goto11, goto110);
SIGNAL current : state := reset;
BEGIN
  PROCESS(clk)
  BEGIN
    IF clk = '1' THEN
      CASE current IS
         WHEN reset =>
            IF x = '1' THEN current <= goto1;
            ELSE current <= reset;  END IF;
         WHEN goto1 =>
            IF x = '1' THEN current <= goto11;
            ELSE current <= reset;   END IF;
         WHEN goto11 =>
            IF x = '1' THEN current <= goto11;
            ELSE current <= goto110;  END IF;
         WHEN goto110 =>
            IF x = '1' THEN current <= goto1;
            ELSE current <= reset;  END IF;
      END CASE;
    END IF;
  END PROCESS;
  z <='1' WHEN current = goto110 ELSE '0';
END behavioral;
```

- Entity and architecture for interface and operation
- A single process includes a case statement
- Statements in a process statement execute sequentially

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110_detector.top_down_design

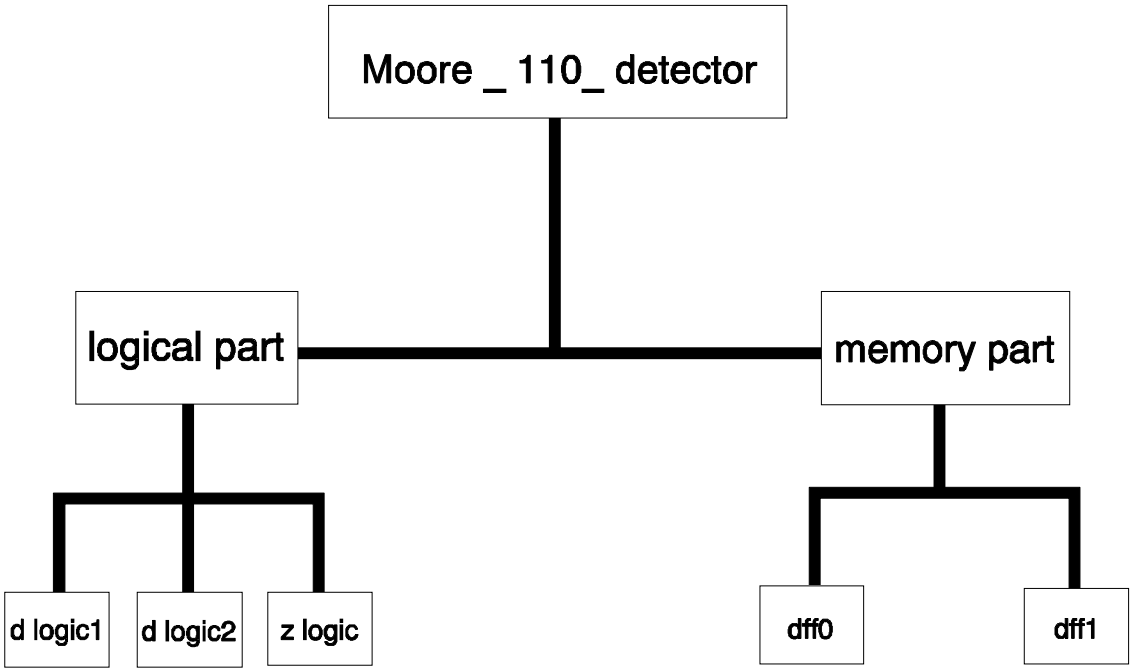

- Partition design to available components

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110_...top_down_...overall_structure

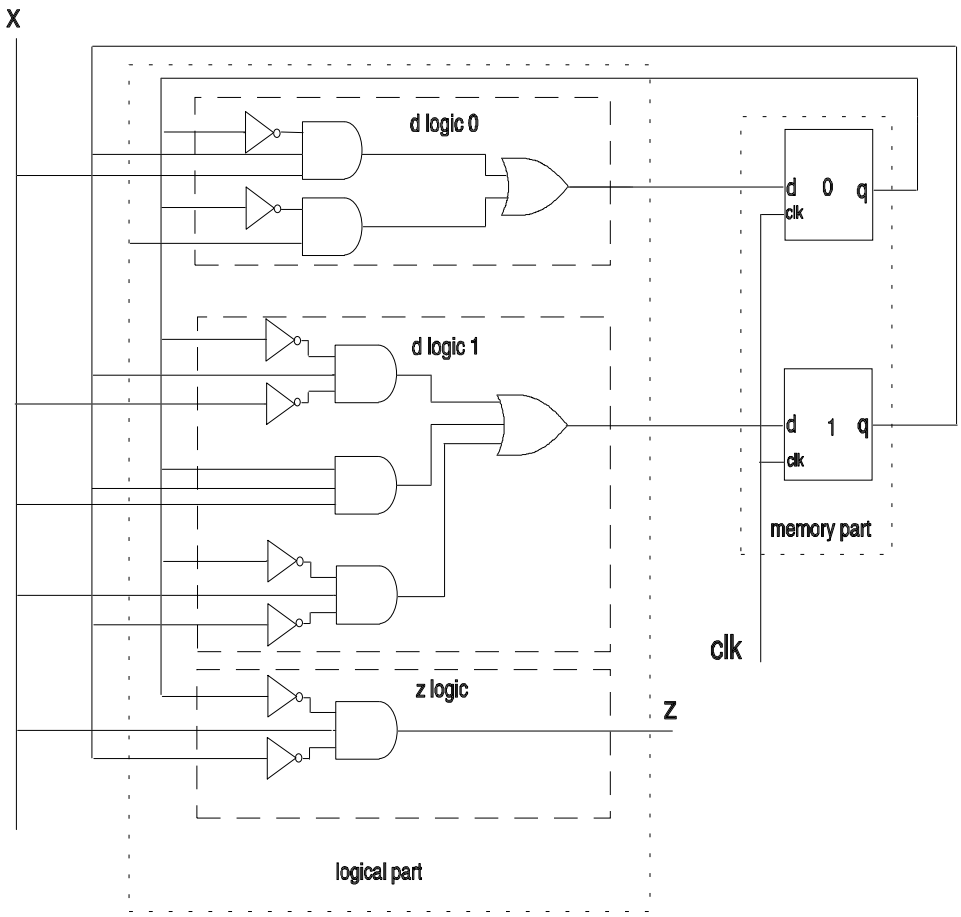

- Logic circuit for the sequence detector
- Three logical functions are used

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110_...top_down...available_components

```
ENTITY dff IS
  PORT(d : IN BIT; clk : IN BIT; q : OUT BIT);
END dff;
--
ARCHITECTURE dataflow OF dff IS
BEGIN
  b:BLOCK (clk = '1' AND NOT clk'STABLE)
  BEGIN
    q <= GUARDED d AFTER 11 NS;
  END BLOCK;
END dataflow;
```

- Available parts include DFF, and f, g, and z logical functions
- VHDL Entity & Architecture for each unit is shown

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110_...top_down...available_components

```
ENTITY logicfunction_f IS
  PORT (i1, i2, i3 : IN BIT; o1 : OUT BIT);
END logicfunction_f;
--
ARCHITECTURE dataflow OF logicfunction_f IS
BEGIN
  o1 <= ((NOT i1) AND i2) OR ((NOT i2) AND i1 AND i3) AFTER 8 NS;
END dataflow;

ENTITY logicfunction_g IS
  PORT (i1, i2, i3 : IN BIT; o1 : OUT BIT);
END logicfunction_g;
--
ARCHITECTURE dataflow OF logicfunction_g IS
BEGIN
  o1    <=      (i2 AND (NOT i1) AND (NOT i3)) OR (i2 AND i1 AND i3) OR
                ((NOT i2) AND (NOT i1) AND i3) AFTER 8 NS;
END dataflow;

ENTITY logicfunction_z IS
  PORT (i1, i2, i3 : IN BIT; o1 : OUT BIT);
END logicfunction_z;
--
ARCHITECTURE dataflow OF logicfunction_z IS
BEGIN
  o1 <= (i2 AND (NOT i1) AND (NOT i3)) AFTER 8 NS;
END dataflow;
```

- VHDL Entity & Architecture for logical functions

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110...top_down_...first_level_wiring

```
ENTITY logical_part IS
  PORT (x, q0_in, q1_in : IN BIT; d0_out, d1_out, z_out  : OUT BIT);
END logical_part;
--
ARCHITECTURE structural OF logical_part IS
  COMPONENT  c1 PORT (i1, i2, i3 : IN BIT ; o1 : OUT BIT);
  END COMPONENT;
  FOR d_logic0 : c1 USE ENTITY WORK.logicfunction_g (dataflow);
  COMPONENT   c2 PORT (i1, i2, i3 : IN BIT; o1 : OUT BIT);
  END COMPONENT;
  FOR d_logic1 : c2 USE ENTITY WORK.logicfunction_f (dataflow);
  COMPONENT   c3 PORT(i1,i2,i3 : IN BIT; o1 : OUT BIT);
  END COMPONENT;
  FOR z_logic :c3 USE ENTITY WORK.logicfunction_z(dataflow);
BEGIN
  d_logic0: c1 PORT MAP(q0_in,q1_in,x,d0_out);
  d_logic1: c2 PORT MAP(q0_in,q1_in,x,d1_out);
  z_logic : c3 PORT MAP(q0_in,q1_in,x,z_out);
END structural;
```

- Wiring the logical part
- Statements in architecture execute concurrently

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110...top_down_...first_level_wiring

```
ENTITY memory_part IS
  PORT(d0_in,d1_in,clk : IN BIT;q0_out,q1_out : OUT BIT);
END memory_part;
--
ARCHITECTURE structural OF memory_part IS
  COMPONENT  m
    PORT(d : IN BIT; clk : IN BIT; q : OUT BIT);
  END COMPONENT;
  FOR dff0, dff1 : m USE ENTITY WORK.dff (dataflow);
BEGIN
  dff0 : m PORT MAP (d0_in, clk, q0_out);
  dff1 : m PORT MAP (d1_in, clk, q1_out);
END structural;
```

- Wiring memory part
- Memory part consists of two flip-flops
- Statements in Architecture execute concurrently

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110...top_down_...wiring_complete_system

```
ARCHITECTURE structural OF moore_110_detector IS
  COMPONENT
    l PORT (x, q0_in, q1_in : IN BIT; d0_out, d1_out, z_out : OUT BIT);
  END COMPONENT;
  FOR lpart : l USE ENTITY WORK.logical_part (structural);
  COMPONENT
    m PORT (d0_in, d1_in, clk : IN BIT; q0_out, q1_out : OUT BIT);
  END COMPONENT;
  FOR mpart : m USE ENTITY WORK.memory_part(structural);
  SIGNAL conn0, conn1, conn2, conn3 : BIT;
BEGIN
  lpart : l PORT MAP (x, conn0, conn1, conn2, conn3, z);
  mpart : m PORT MAP (conn2, conn3, clk, conn0, conn1);
END structural;
```

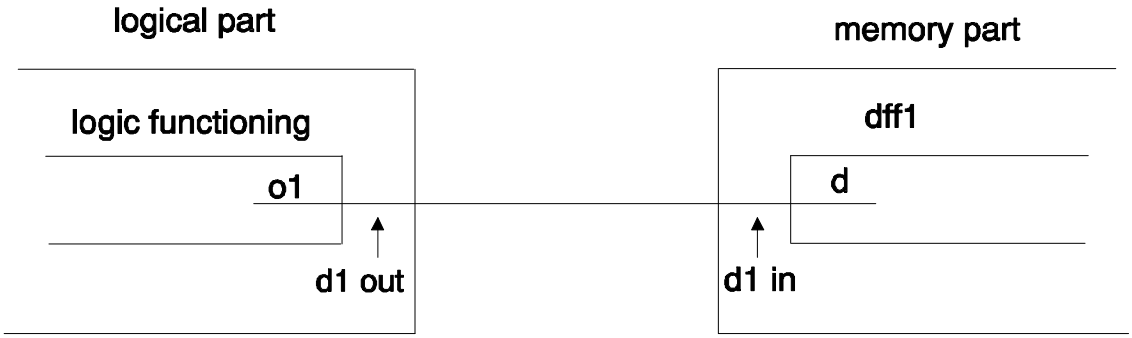

- Same entity as declared
- Use structural instead of behavioral architecture

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110_detector.testbench

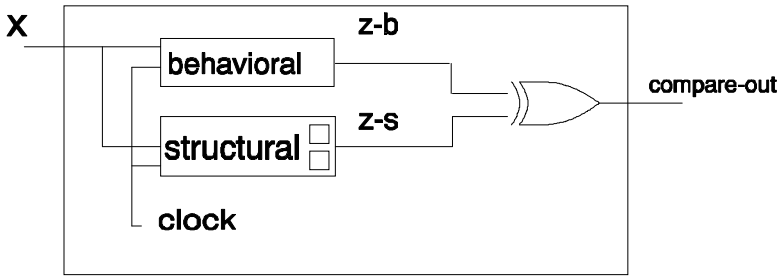


```
ENTITY  moore_test IS   END moore_test;
--
ARCHITECTURE input_output OF moore_test IS
  COMPONENT comp1      PORT (x, clk : IN BIT; z : OUT BIT);
  END COMPONENT;
  FOR c1 : comp1 USE ENTITY WORK.moore_110_detector (behavioral);
  FOR c2 : comp1 USE ENTITY WORK.moore_110_detector (structural);
  SIGNAL x_in, clock, z_beh, z_struct, compare_out : BIT;
BEGIN
  x_in <= '0',  '1' AFTER 500 NS,
                '0' AFTER 900 NS,          '1' AFTER 1100 NS,
                '0' AFTER 1300 NS,         '1' AFTER 1500 NS,
                '0' AFTER 1900 NS,         '1' AFTER 2100 NS,
                '0' AFTER 2300 NS,         '1' AFTER 2500 NS;
  clock <= NOT clock AFTER 100 NS WHEN NOW < 3000 NS ELSE clock;
  c1 : comp1 PORT MAP (x_in, clock, z_beh);
  c2 : comp1 PORT MAP (x_in, clock, z_struct);
  compare_out <= z_beh XOR z_struct;
END input_output;
```

- A testbench tests and compares two architectures

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110_detector.data_generation

```
PROCEDURE   serial_data_generation
(SIGNAL target : OUT BIT; int : IN INTEGER; t : IN TIME) IS
   VARIABLE i : INTEGER;
   VARIABLE bit_val : BIT;
   VARIABLE current : TIME :=100 NS;
BEGIN
  i := int;
  WHILE i >0 LOOP
    IF (i MOD 2 = 1) THEN
      bit_val := '1';
    ELSE
      bit_val := '0';
    END IF;
    target <= TRANSPORT bit_val AFTER current;
    current := current + t;
    i := i/2;
  END LOOP;
END serial_data_generation;
```

- Procedure is a sequential body
- It takes zero real time to execute the entire procedure

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110_detector.procedural_test

```
ARCHITECTURE procedural OF moore_test IS
  PROCEDURE serial_data_generation
  (SIGNAL target : OUT BIT; int : IN INTEGER; t : IN TIME) IS
     VARIABLE i : INTEGER;
     VARIABLE bit_val : BIT;
     VARIABLE current : TIME :=100 NS;
  BEGIN
    i := int;
    WHILE i > 0 LOOP
      IF (i MOD 2 = 1) THEN  bit_val :='1';
      ELSE  bit_val := '0';
      END IF;
      target <= TRANSPORT bit_val AFTER current;
      current:=current + t;
      i := i / 2;
    END LOOP;
  END serial_data_generation;
  COMPONENT comp  PORT (x,clk:IN BIT;z:OUT BIT);  END COMPONENT;
  FOR c1 : comp USE ENTITY WORK.moore_110_detector(structural);
  SIGNAL x_in, clock, z_struct : BIT;
 BEGIN
  serial_data_generation (x_in, 5548, 200 NS);
  clock <= NOT clock AFTER 100 NS WHEN NOW < 3000 NS ELSE clock;
  c1 : comp PORT MAP (x_in, clock, z_struct);
END procedural;
```

- The three statements execute concurrently

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.moore_110_detector.testbench

- Test may be done for various purposes
  - Verify the design
  - Check the delays
  - Find maximum clock speed
  - Compare behavioral & dataflow
  - A testbench can instantiate two versions of a component
  - XOR gates can be used to flag discrepancies

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.other_operators

PREDEFINED OPERATORS

```
     LOGICAL OPERATORS: NOT AND OR NAND NOR XOR
          OPERAND TYPE: BIT BOOLEAN
           RESULT TYPE: BIT BOOLEAN

  RELATIONAL OPERATORS: = / = < <= > >=
          OPERAND TYPE: any type
           RESULT TYPE: BOOLEAN

  ARITHMETIC OPERATORS: + - * / **
                      : MOD REM ABS
          OPERAND TYPE: INTEGER REAL physical
           RESULT TYPE: INTEGER REAL physical

CONCATENATION OPERATOR: &
          OPERAND TYPE: array of any type
           RESULT TYPE: array of any type
```

- Operators exist for logical and arithmetic operations
- Concatenation operator produces array

© Zainalabedin Navabi, 1994

© Zainalabedin Navabi, 1994

VHDL_Overview.conclusions

1. Outline: Introduction, Organization, Outline

2. Overview: Behavioral description, Using process statements, Top-down design, Using available components, Wiring predefined components, Wiring from bottom to top, Generation of testbench data, Using procedures

3. VHDL_Timing: Modeling requirements, Objects & classes, Signals & variables, Concurrent & sequential assignments, Events, transactions & delta delays, Delay modeling, Sequential placement of transactions, Conventions

4. Structural_Description_of_Hardware: Wiring parts into larger designs, Start with primitives, Wire gates into general purpose components, Use iterative constructs, Generate testbenches, Show binding alternatives, Use gate-based components for a larger design

5. Design_Organization: Subprograms, Packaging, Parameter specification, Parametrization, Top level configuration, Design libraries, A complete example

6. Utilities_for_high_level_descriptions: Language aspects, Types, Over loading subprograms operators, Predefined Attributes, User defined attributes

7. Dataflow: Constructs for dataflow descriptions, Multiplexing and clocking, Multiple assignments, State machines, Open collector gates, A complete dataflow example, Load dependent timing

8. Behavioral_Descriptions: Constructs for sequential descriptions, Assertion for behavioral checks, Handshaking constructs, Timing control, Formatted I/O, MSI parts, A complete MSI based design

9. STANDARDS: MVL9: logic value system, Logic type, Operators, Conversions; VHDL'93: Operators, Delay model, Instantiation, Binding, Attributes, Signal assignments, Report, Postponed process

© Zainalabedin Navabi, 1994

ERROR: undefined
OFFENDING COMMAND: x

STACK: